

Name: _____

Edexcel_EMF_Old

Mark Scheme

Date:

Time:

Total marks available:

Total marks achieved: _____

Mark Scheme

Q1.

Question Number	Answer	Mark
	C	1

Q2.

Question Number	Answer	Mark
	D	1

Q3.

Question Number	Answer	Mark
	<p>p.d. is electrical energy(/coulomb) transferred between two points/electrical energy transformed/converted to other forms (1)</p> <p>e.m.f is the energy(/coulomb) supplied to a circuit/given to the charge/energy output of the cell (1)</p> <p>(full credit if wording implies emf as electrical energy source and pd as electrical energy sink)</p> <p>If neither mark scored but reference to energy/charge is made scores 1 mark only</p>	2
Total for question		2

Q4.

Question Number	Answer	Mark
	<p>Either</p> <p>Show that with $R=0$ then $\mathcal{E} = Ir$ (1)</p> <p>A small r would result in a large current (1)</p> <p>Or</p> <p>If there is a short circuit (1)</p> <p>Limit current in external circuit (1)</p>	2

Q5.

Question Number	Answer	Mark
	Use of $V = IR$ Use of lost volts = emf – terminal pd Or use of total resistance – 6.6Ω (quoting $\varepsilon = I(R + r)$ or $\varepsilon = V + Ir$ gets both marks) Internal resistance = $0.54\ \Omega$ (rounding and different methods all give $0.5\ \Omega$ to 1 sig. fig.)	(1) (1) (1)
	<u>Example of calculation</u> $V = 0.21\ \text{A} \times 6.6\ \Omega = 1.39\ \text{V}$ $Ir = 1.5\ \text{V} - 1.39\ \text{V} = 0.11\ \text{V}$ $r = 0.11\ \text{V} \div 0.21\ \text{A} = 0.54\ \Omega$	3
	Total for question	3

Q6.

Question Number	Answer	Mark
(i)	Attempts to draw line of best fit to y-axis $\mathcal{E} = 6.1 - 6.3\ \text{V}$	(1) (1) 2
(ii)	Attempts to find gradient Or use of $E = V + Ir$ using their E and corresponding values of V and I from their graph $r = 1.5\ \Omega$ to $1.6\ \Omega$	(1) (1) 2

Q7.

Question Number	Answer	Mark
(a)	State ($V = E - Ir$) (1) Correct substitution (1) p.d. = 11V (1) OR Use of ($V = Ir$) to attempt to find lost volts (1) Subtraction from E (1) p.d. = 11V (1) OR Use of $E = I(R+r)$ to attempt to find R (1) Use of $V = IR$ with the value of R calculated (1) p.d. = 11V (1) <u>Example of calculation</u> $V = 12 \text{ V} - 3 \times 10^{-3} \Omega \times 400 \text{ A}$ p.d. = 10.8 V	3
(b)	To prevent large energy dissipation / wire heating up / wire melting / large pd across the wires OR to allow a large current (1) Resistance of cable low (1) (cross-sectional) area large [Not surface area] (1) [Reverse argument in terms of a thin wire acceptable for all points]	3
Total for question		6

Q8.

Question Number	Answer	Mark
(a)	Negative gradient (accept curve)	(1)
	Straight line (dependent on first marking point)	(1)
	Reference to terminal p.d. = e.m.f. – ‘lost volts’ Or $V = \varepsilon - Ir$	(1)
	Intercept on V axis = ε Or Intercept on y axis = ε Or $\varepsilon =$ value of V on graph when $I = 0$ (accept from labelled graph)(mark not awarded if line passes through origin)	(1)
	Gradient = $-r$ Or magnitude of gradient is r (accept gradient = $-r$ marked on graph)	(1)
		5
*(b)	(QWC – Work must be clear and organised in a logical manner using technical wording where appropriate)	
	Ammeter explanation:	
	If ammeter has resistance, current decreased but doesn't affect the determination because current through cell/ r is measured	(1)
	Or doesn't affect the determination because the voltmeter measures the terminal p.d. for that current	(1)
	OR	
	The resistance of the ammeter contributes to the load/circuit/total resistance	(1)
	Values of p.d. corresponding to given values of current will be unchanged	(1)
Voltmeter explanation:		
If voltmeter has smaller resistance it would draw current measured current not current through cell/ r	(1)	
		(1)
		4
	Total for question	9

Q10.

Question Number	Answer	Mark
(a)(i)	resultant e.m.f. = $15 \text{ V} - 7.6 \text{ V} = 7.4 \text{ V}$	(1) 1
(a)(ii)	Total resistance = $0.65 \Omega + 0.050 \Omega = 0.70 \Omega$	(1) 1
(a)(iii)	Use of $I = V/R$ $I = 11 \text{ A}$ (allow ecf for values from (i) & (ii)) (22.6 V gives 32.3 A) <u>Example of calculation</u> $I = 7.4 \text{ V} / 0.7 \Omega$ $I = 10.6 \text{ A}$	(1) (1) 2
(b)(i)	Use of p.d. across series resistance = $4.3 \text{ A} \times 0.65 \Omega$ Subtraction of calculated p.d. value from 15 V Terminal p.d. = 12.2 (V) [no ue] OR Use of p.d. across internal resistance of battery = $4.3 \text{ A} \times 0.05 \Omega$ Addition of calculated p.d. value to 12 V Terminal p.d. = 12.2 (V) [no ue] <u>Example of calculation</u> p.d. across internal resistance = $4.3 \text{ A} \times 0.65 \Omega = 2.8 \text{ V}$ Terminal p.d. = $15 \text{ V} - 2.8 \text{ V}$ Terminal p.d. = 12.2 V	(1) (1) (1) 3 (1) (1) (1)
(b)(ii)	Use of $P = VI$ Rate of energy = 65 W <u>Example of calculation</u> Power = $15 \text{ V} \times 4.3 \text{ A}$ Power = 64.5 W	(1) (1) 2
(b)(iii)	Use of $P = I^2 r$ (to find wasted power for internal resistance, series resistance or total resistance) (allow ecf from (a)(ii)) Subtraction of this value from answer to (b)(ii) (allow ecf) Efficiency = 80% (allow ecf) Or $12 \text{ V} \times 4.3 \text{ A}$ (for useful power = 51.6 W) Use of ratio of useful power/total power Efficiency = 80% (efficiency = ratio of emfs leading to 80% scores 3 marks) <u>Example of calculation</u> Wasted power = $(4.3 \text{ A})^2 \times 0.7 \Omega = 13 \text{ W}$ Efficiency = $(65 - 13)/65$ Efficiency = 80%	(1) (1) (1) 3 (1) (1) (1)
	Total for question	12

Question Number	Answer	Mark
(a)	Plot of graph Check points, 4 correct 2 marks, 3 correct 1 mark Line of best fit to include 0,0.6 and 0.52,0 (1)	3
(b)(i)	Use of $V = 0.43 \text{ V}$ in $P = VI$ (1) ecf values for incorrect best fit line $P = 0.17 \text{ W}$ (1) Example of calculation $P = 0.4 \text{ A} \times 0.43 \text{ V}$ $P = 0.172 \text{ W}$	2
(b)(ii)	Value of e.m.f. is when the current is zero (1) No 'lost' volts OR no energy loss (1) OR $E = V + Ir$ $I = 0, E = V$	2
(b)(iii)	Identifies current in circuit (1) ecf values for incorrect best fit line Finds 'lost volts' (1) $r = 0.24 \Omega$ (1) Example of calculation $r = (0.52 \text{ V} - 0.40 \text{ V}) \div 0.50 \text{ A}$ $r = 0.24 \Omega$	3
(c)	Graph of similar shape as in (a) but initially above the first graph (1) ecf values for incorrect best fit line Finishing at 0.52 V, 0.00 A (1)	2
Total for question		12